

Learning Intentions

- How to calculate the equivalent resistance in resistors placed in parallel and in series.
- The rules for finding the voltage and current through resistors in complex circuits.

Notes and Vocabulary

1. Electric load is the part of a circuit that consumes electric power.
2. The equivalent resistance is the "total" resistance of a circuit.
3. In series, the equivalent resistance is found by adding resistances according to the formula




$$R_{eq} = \sum R_i = R_1 + R_2 + \dots$$

- a. If R_1 is 150Ω and R_2 is 100Ω , what is the equivalent resistance of the circuit above?

$$R_{eq} = R_1 + R_2 = 150 \Omega + 100 \Omega = 250 \Omega$$

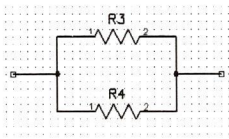4. In parallel, the equivalent resistance is found according to the formula



$$\frac{1}{R_{eq}} = \sum \frac{1}{R_i} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$$

- a. If R_3 is 150Ω and R_4 is 100Ω , what is the equivalent resistance of the circuit above?

$$\frac{1}{R_{eq}} = \frac{1}{R_3} + \frac{1}{R_4} = \frac{1}{150 \Omega} + \frac{1}{100 \Omega} = \frac{1}{60 \Omega} \Rightarrow R_{eq} = \left[\frac{1}{60 \Omega} \right]^{-1} = 60 \Omega$$

5. There are 3 important rules for resistor circuits

- a. Ohm's Law (from last class)

$$V = I \times R$$

↗ current (I)
 ↘ resistance (R)
 ↙ voltage (V)


- b. Kirchhoff's Voltage Rule:

- i. The Theory of Conservation of Energy says that the voltage increase at the battery is

equal to the voltage decrease through the load.

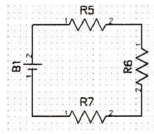ii. This law is also known as Kirchoff's Loop rule, because it states that the


voltage changes around a circuit add to zero.



$$V_{B1} - V_{R5} - V_{R6} - V_{R7} = 0$$


c. Kirchoff's Junction Rule:

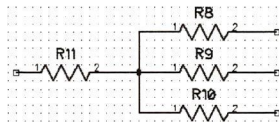i. Electric current (I, in Amps) is the flow of electrons, so the total flow of electrons into a node (or junction) has to equal the total flow of electrons out of of the node.



$$I_{R1} = I_{R8} + I_{R9} + I_{R10}$$

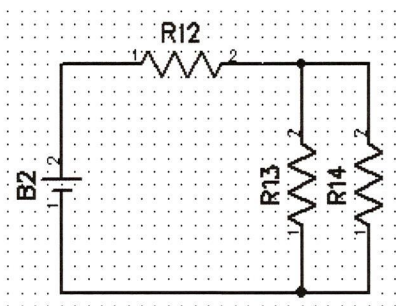6. In high school, you are expected to solve circuit problems by finding the equivalent resistance.




Look at R13 and R14 to start (start with parallel)

~~$$\frac{1}{R_{1314}}$$~~

$$\frac{1}{R_{eq1}} = \frac{1}{R_{13}} + \frac{1}{R_{14}} = \frac{1}{50\Omega} + \frac{1}{400\Omega}$$


$$R_{eq1} = \left[\frac{1}{50\Omega} + \frac{1}{400\Omega} \right]^{-1} = 44\Omega$$

The circuit then simplifies

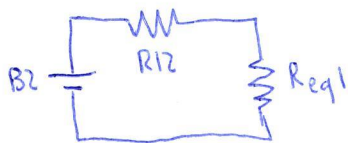

$$R_{eq2} = R_{12} + R_{eq1} = 75\Omega + 44\Omega = 119\Omega$$

And the circuit becomes

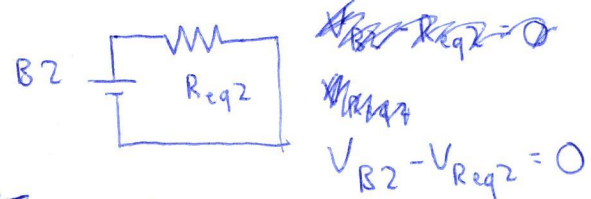

~~$$V_{Req2} = V_{B2} = 5.0V$$~~

$$V_{Req2} = V_{B2} = 5.0V$$


~~$$I_{Req2} = \frac{V_{Req2}}{R_{eq2}} = \frac{5.0V}{119\Omega} = 0.042A$$~~

$$I_{Req2} = \frac{V_{Req2}}{R_{eq2}} = \frac{5.0V}{119\Omega} = 0.042A$$


This is a lengthy and tedious process. We will use computers instead.

Continued →

We now know everything about circuit 3

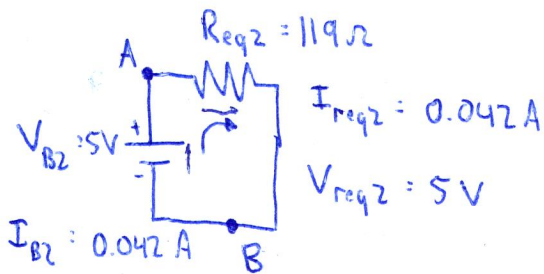

We can use this to help solve circuit 2

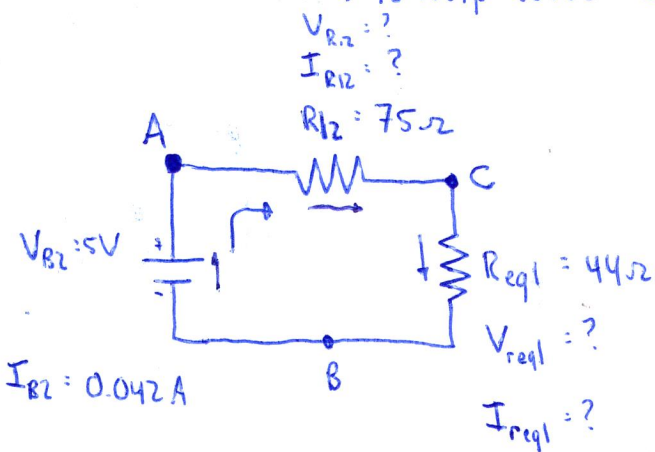

Looking at Node A

$$I_{B2} - I_{R12} = 0$$

$$I_{R12} = I_{B2} = 0.042A$$

Looking at Node B

$$I_{Req1} - I_{B2} = 0$$

$$I_{Req1} = I_{B2}$$


Applying Ohm's Law

$$V_{R12} = I_{R12} \times R_{12} = 0.042A \times 75\Omega = 3.2V$$

$$V_{Req1} = I_{Req1} \times R_{eq1} = 0.042A \times 44\Omega = 1.8V$$

$$3.2V + 1.8V = 5.0V = V_{B2}$$

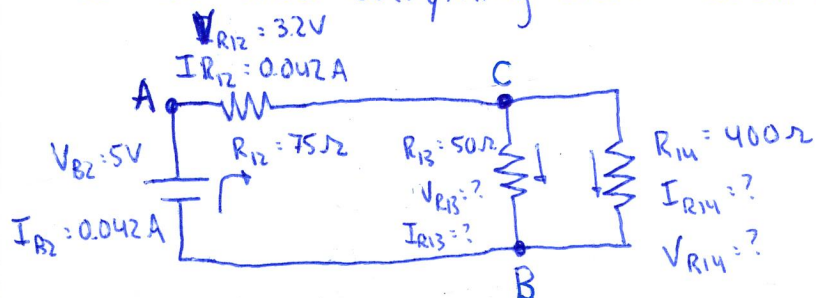We now know everything about circuit 2, and use it to solve circuit 1



Looking at the loop through B2, R12, and R13

$$V_{B2} - V_{R12} - V_{R13} = 0$$

$$V_{R13} = V_{B2} - V_{R12} = 5V - 3.2V = 1.8V$$

Looking at the loop through B2, R12, and R14 OR the loop through R13 and R14

$$V_{B2} - V_{R12} - V_{R14} = 0$$

$$V_{R13} - V_{R14} = 0$$

$$V_{R14} = V_{B2} - V_{R12} = 5V - 3.2V = 1.8V$$

$$V_{R14} = V_{R13} = 1.8V$$

All this work above (↑) can be avoided by recognizing that $V_{R13} = V_{R14} = V_{req1}$ because they all have the same voltage drops from Node C to Node B.

To find current, we use Ohm's Law

$$I_{R13} = \frac{V_{R13}}{R_{13}} = \frac{1.8V}{50\Omega} = 0.036A$$

$$I_{R14} = \frac{V_{R14}}{R_{14}} = \frac{1.8V}{400\Omega} = 0.0045A$$

$$I_{R13} + I_{R14} = 0.041A = I_{req1}$$

We have now solved the whole circuit.